AlGaInP APC Visible Laser Diode

ADL-65052SA4

6-2D-LD65-099_Rev.01

650nm 5mW I D

By converting the external APC circuit board into an ASIC, we package the APC circuit into a traditional TO-can together with the laser chip. From now on, single package APC function included laser diode is realized. Powered with Arima's proprietary APC LASER DIODE TM technology, ADL-65052SA4 is your perfect solution for the stable light power output, compact size, high brightness laser light source.



Features

- 1. 650nm 5mW 50°C high reliable operation
- 2. Saving space and cost of laser module
- Voltage driven LD, easy to use
- 4. Highly stable laser output power
- 5. Strong reverse bias protection
- 6. High ESD sustainability
- 7. Stable output power vs. supply voltage from 2.5V to 6.0V.
- 8. Light-fuse: automatic shutdown when output power over the limit

Applications

- 1. Industry: laser level, illumination, meter, scanner, detector
- 2. Consumer: pointer light, sweeper, TV game lighting
- 3. Health: special wavelength light source

Absolute maximum ratings

Parameter	Symbol	Rating	Unit
Power supply voltage	V _{cc}	2.5~6.0	V
Laser optical output power	Po	7.0	mW
Operation temperature	T _{opr}	-10 ~ +50	°C
Storage temperature	T _{stg}	-40 ~ +85	°C

Electrical and optical characteristics (T_c=25 °C)

Parameter	Symbol	Min.	Тур.	Max.	Unit	Conditions	
Wavelength	λ	645	656	660	nm	Po=5mW	
Operation current	l _{op}	-	20	25	mA	Po=5mW	
Variable resistor	VR	3	8	20	ΚΩ	Vcc=3V	
Parallel divergence angle	θ//	6	9	12	Deg	Po=5mW	
Perpendicular divergence angle	θ_{\perp}	24	30	32	Deg		
Parallel FFP deviation angle	Δ θ//	-3.0	0	+3.0	Deg		
Perpendicular FFP deviation angle	Δ θ μ	-3.0	0	+3.0	Deg		
Emission point accuracy	Δ xΔ yΔ z	-80	0	+80	um	-	
Power-Temp stability (25~50°C)	Δ P _{oT}	-20	-10	0	%	Po=5mW, Vcc=3.0V	
Power-Vcc stability (6.0~3.0V)	Δ P _{oV}	-15	-10	0	%	Po=5mW,Temp=25°C	
Power-Vcc stability (3.0~2.5V)	Δ P _{oV}	-15	-10	0	%	Po=5mW,Temp=25°C	

^{*} Effective heat sink is recommended on 6V case due to extra heat



PHONE: 886-3-4699800 | FAX: 886-3-4699600 E-MAIL: Ldsales@arimalasers.com | www.arimalasers.com





6-2D-LD65-099_Rev.01

650nm 5mW LD

Block Diagram:


- Traditional LD needs to connect an external APC circuit board for the constant power operation. The VR (variable resistor) is used to adjust the laser output to a desired target power.
- ADL-65052SA4 consists an APC IC inside the TO-3.3mm package, and leaves the VR outside for adjusting the optical output power.
- Oscillation Damper is recommended for stabilizing the optical output power.
- 4. Battery reverse protection is recommended for protecting the APC Circuit.

- 1. Vcc
- 2. GND
- 3. VR

Outline Dimension & Pin Assignment:

- 1. Vcc
- 2. GND

3. VR

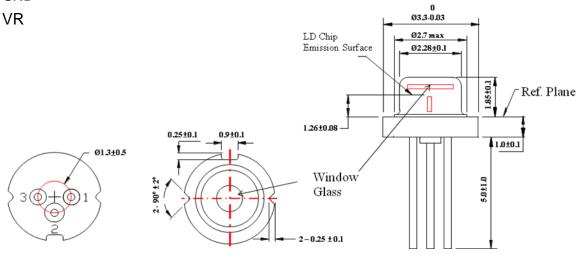

• Precautions

- * To protect laser from overdriving condition, setting VR to maximum value before you turn on Vcc can minimized the laser output power.
- * Do not operate the device above the maximum rating condition, even momentarily. It may cause unexpected permanent damage to the device.
- * Semiconductor laser device is very sensitive to electrostatic discharge. High voltage spike current may change the characteristics of the device, or malfunction at any time during its service period. Therefore, proper measures for preventing electrostatic discharge are strongly recommended.
- * To obtain a stable characteristic and good reliability, the effective heat sink is necessary. So it is recommended that always apply proper heat sink before the device is operating.
- * Do not look into the laser beam directly by bare eyes. The laser beam may cause severe damage to human eyes.

